
## 1 ModelSim waveforms

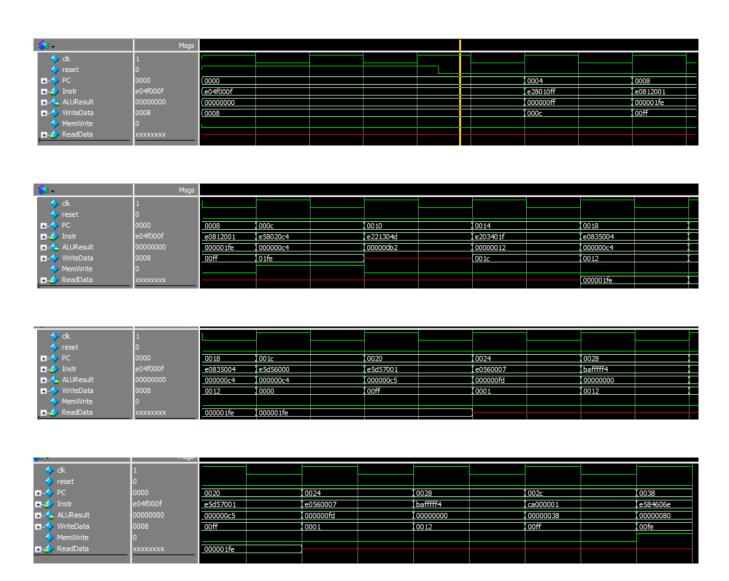

The last operation is: STR R6, [R4, #110] because SUBS R0, R6, R7 creates a positive number bigger than 0. Therefore we branch to 'HERE'. This operation stores the value of R6 at address  $mem[128] \Rightarrow mem[128] = 0xFE$ .

### 2 Schematics

#### 2.1 Single-cycle ARM processor

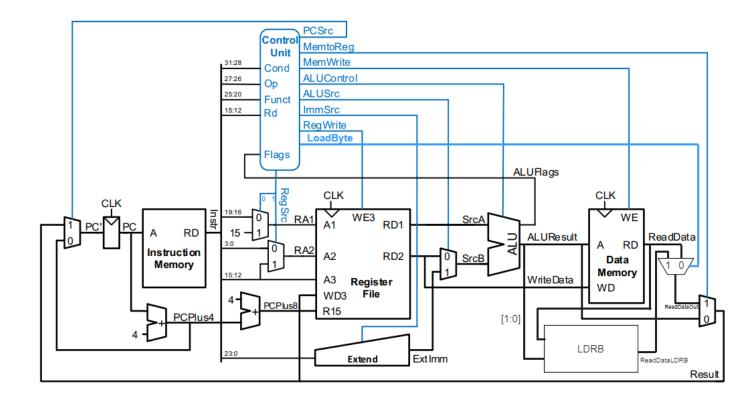


Figure 1: Marked up single-cycle processor

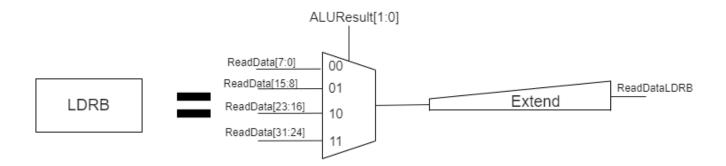


Figure 2: Equivalent schematic of LDRB

### 2.2 ALU

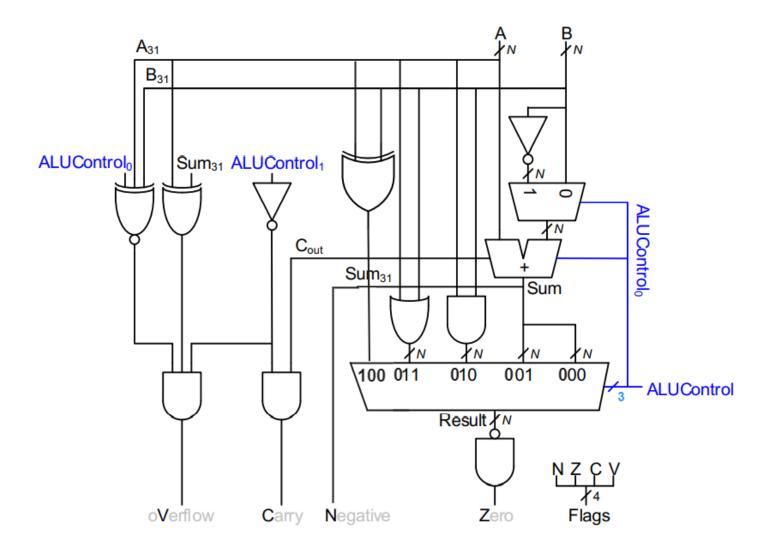


Figure 3: Marked up ALU

### 3 Decoder tables

$Funct_2$	Ор	Funct <sub>5</sub>	Funct <sub>0</sub>	Туре	Branch	MemtoReg	MemW	ALUSrc	ImmSrc	RegW	RegSrc	ALUOP	LoadByte
Х	00	0	X	DP Reg	0	0	0	0	XX	1	00	1	0
Х	00	1	Х	DP Imm	0	0	0	1	00	1	X0	1	0
0	01	Х	0	STR	0	X	1	1	01	0	10	0	0
Х	01	Х	1	LDR	0	1	0	1	01	1	X0	0	0
Х	10	X	X	В	1	0	0	1	10	0	X1	0	0
1	01	Х	1	LDRB	0	1	0	1	01	1	X0	0	1

Figure 4: Main Decoder

Notes **ALUOp** Funct<sub>4:1</sub> (cmd) Funct<sub>o</sub> (S) ALUControl<sub>2:0</sub>  $FlagW_{1:0}$ Х Not DP Х ADD SUB AND ORR **EOR** 

Figure 5: Alu decoder

# 4 SignalTap waveforms

I couldn't get the clock nor the reset to work. Hence, the constant value 0 for both of them.

Туре	Alias	Name	Τ	-3	-2	-1 (	) 1
*		arm:arm clk	0				
*		arm:arm reset	0				
•		arm:arm PC[310]	C	35E7D100h	X 35E7D104h	35E7D108h	35E7D10Ch
•		⊞ arm:arm Instr[310]		E04F000Fh	E28010FFh	E0812001h	E58020C4h
-		⊞ arm:arm ALUResult[310]		00000000h	000000FFh	000001FEh	000000C4h
•		⊕ arm:arm WriteData[310]		35E7D108h	35E7D10Ch	000000FFh	000001FEh
*		arm:arm MemWrite	0				
-		⊞ arm:arm ReadData[310]			0000000h		000001FEh

Name	l lo		1	2	3	4
arm:arm clk	0					
arm:arm reset	0					
arm:arm PC[310]	$\circ$	35E7D10Ch	35E7D110h	35E7D114h	35E7D118h	X
arm:arm Instr[310]		E58020C4h	E221304Dh	E203401Fh	E0835004h	X
arm:arm ALUResult[310]		000000C4h	000000B2h	00000012h	X	000000C4h
⊞ arm:arm WriteData[310]		000001FEh	0000000h	35E7D11Ch	00000012h	X
arm:arm MemWrite	0					
⊕ arm:arm ReadData[310]		000001FEh	0000	0000h	X	

Name	4		5	б	7	8
arm:arm clk	0					
arm:arm reset	0					
⊕ arm:arm PC[310]	$\circ$	35E7D11Ch	35E7D120h	35E7	D124h X 35E70	)128h
⊕ arm:arm Instr[310]		E5D56000h	E5D57001h	E056	0007h X BAFFE	FF4h
⊕ arm:arm ALUResult[310]		000000C4h	000000C5h	0000	00FDh X 35E7E	)100h
⊕ arm:arm WriteData[310]		00000000h	000000FFh	0000	0001h X 00000	0012h
arm:arm MemWrite	0					
⊕ arm:arm ReadData[310]		00000	01FEh		00000	0000h

Name	7		9	9	10	
Name	ı'	,	<b>1</b>	7	٩١	
arm:arm clk	0					
arm:arm reset	0					
arm:arm PC[310]	$\circ$	35E7D128h	35E7D12Ch	351	7D138h	35E7D13Ch
⊞ arm:arm Instr[310]		BAFFFFF4h	CA000001h	X E58	34606Eh	
⊞ arm:arm ALUResult[310]		35E7D100h	35E7D138h	X 000	000080h	
⊞ arm:arm WriteData[310]		00000012h	000000FFh	X 000	0000FEh	
arm:arm MemWrite	0					
⊞ arm:arm ReadData[310]		00000	0000h	X 000	0000FEh	